
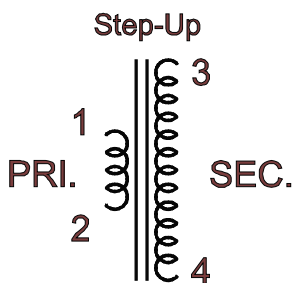



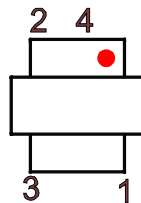
Mini-Transformer Step-Up Application Notes



Top View T1




Top View – PCB hole layout

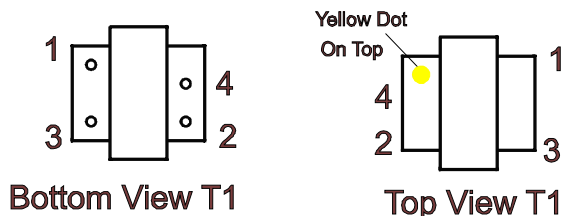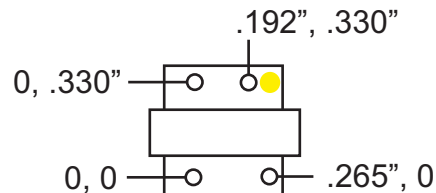


Notice that the primary winding pins 1 & 2 are at the corners.

NOTE: Vcc = +5 VDC

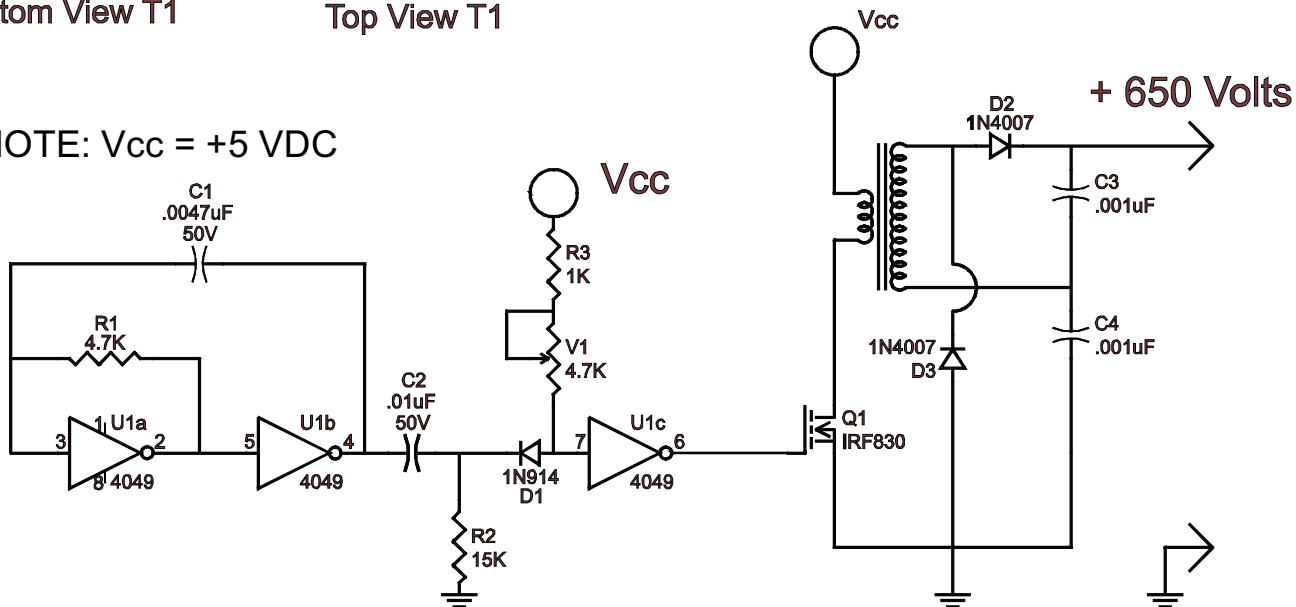

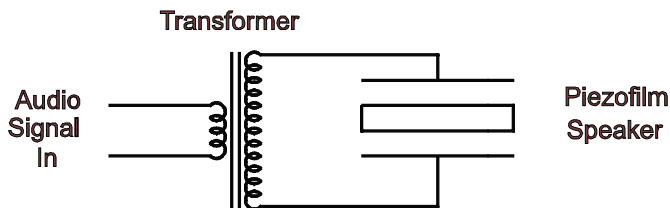This small transformer is capable of outputting 600 volts or more with the simple circuit shown above. The circuit uses a 4049 hex inverter buffer IC to generate a square wave. The 4.7K potentiometer adjusts the width of the pulse. The IRF830 Power Mosfet controls the current to the primary windings of the mini step-up transformer.




An audio signal feed to the primary will step up the voltage enough to power a piezo-film speaker.

Images SI Inc.

109 Woods of Arden Road
Staten Island NY 10312

718.966.3694 Voice 718.966.3695 Fax

Tiny Inverter Transformer

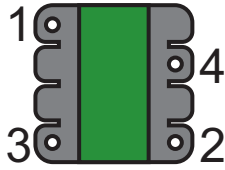

Bottom View of Transformer T1

Important: Inverter transformers are not wired the same as regular transformers. Notice that the primary pins 1 and 2 are at the corners.

Simple Strobe Schematic

